

## Multiplier Design using Booth Encoding

- Booth encoding techniques are used to reduce the number of terms that must be added.
- Various forms of Booth encoding techniques have been proposed.
- As an illustration, we will focus on one variation (usually called modified Booth encoding) that reduces the number of partial products that must be added by a factor of two.
  - The method is valid for signed operands and results.
- We assume that the number of bits,  $n$ , in the multiplier operand  $Y$  is an even number.
- First, consider those cases where  $Y > 0$ . Since the bit  $y_{n-1} = 0$ , we can write:

$$Y = \sum_{k=0}^{n-1} y_k 2^k$$

- Each term in the summation can be written as:

$$y_k 2^k = (2y_k - \frac{1}{2}2y_k)2^k = y_k 2^{k+1} - 2y_k 2^{k-1}$$

- Use the above expansion for the odd- $k$  terms in the summation for  $Y$  to obtain:

$$Y = (y_{n-1}2^n - 2y_{n-1}2^{n-2}) + y_{n-2}2^{n-2} + (y_{n-3}2^{n-2} - 2y_{n-3}2^{n-4}) + y_{n-4}2^{n-4} + \dots \\ + (y_32^4 - 2y_32^2) + y_22^2 + (y_12^2 - 2y_12^0) + y_02^0$$

## Multiplier Design using Booth Encoding - Continued

- Defining  $y_{-1} \equiv 0$  and collecting together terms with the same power of two gives:

$$Y = y_{n-1}2^n + (-2y_{n-1} + y_{n-2} + y_{n-3})2^{n-2} + (-2y_{n-3} + y_{n-4} + y_{n-5})2^{n-4} + \dots \\ + (-2y_3 + y_2 + y_1)2^2 + (-2y_1 + y_0 + y_{-1})2^0$$

- The first term drops out since  $y_{n-1} = 0$ . Define a new set of coefficients  $z_k$  for  $k = \text{even \#}$ :  $z_k \equiv -2y_{k+1} + y_k + y_{k-1}$ , for  $k = 0, 2, 4, \dots, n-2$
- Then, we can write expressions for  $Y$  and the product,  $P = XY$ , in terms of  $z_k$  as:

$$Y = \sum_{\substack{k=0 \\ (k \text{ even})}}^{n-2} z_k 2^k, \quad P = XY = \sum_{\substack{k=0 \\ (k \text{ even})}}^{n-2} (z_k X) 2^k$$

- Notice what this says: We have to generate and sum only  $n/2$  partial products  $z_k X$ , which is approximately half of the original number of partial products  $y_k X$  (remember that we had to prepend 1 or 2 additional 0s to  $Y$ ). This represents a considerable savings in the required hardware. The only mitigating factor is that each partial product is slightly more complex to generate. Since each  $z_k$  depends on the values of 3 adjacent multiplier bits ( $y_{k+1}$ ,  $y_k$  and  $y_{k-1}$ ), there are 8 possible cases to consider. The corresponding value of  $z_k$  in each of the 8 cases is shown on the following page.
- It can be shown that the above results also hold for the case where the  $Y$  operand is negative.

## Multiplier Design using Booth Encoding - Continued

- Using the equation for  $z_k$ , we obtain the following table of the 8 possible cases:

$y_{k+1}$	$y_k$	$y_{k-1}$	$z_k = -2y_{k+1} + y_k + y_{k-1}$
-----	-----	-----	-----
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	2
1	0	0	-2
1	0	1	-1
1	1	0	-1
1	1	1	0

## 8-bit by 8-bit Booth Multiplier Design

- For an 8x8 multiplier design, we will generate 4 partial products (call them a, b, c and d):
  - Negative partial products  $-X$ ,  $-2X$  can be implemented as a one's complement plus 1 to the LSB position.
  - Multiplication by 2 (for  $2X$ ,  $-2X$ ) can be implemented as a shift left by one bit position.
  - The 9-bit partial products must be sign-extended to 16 bits

$$\begin{array}{rcl} k = 0: & y_1 & y_0 & y_{-1} & \Rightarrow & a_8 & a_8 & a_8 & a_8 & a_8 & a_8 & a_8 & a_8 & a_7 & a_6 & a_5 & a_4 & a_3 & a_2 & a_1 & a_0 \\ k = 2: & y_3 & y_2 & y_1 & \Rightarrow & b_8 & b_8 & b_8 & b_8 & b_8 & b_8 & b_7 & b_6 & b_5 & b_4 & b_3 & b_2 & b_1 & b_0 & & u_0 \\ k = 4: & y_5 & y_4 & y_3 & \Rightarrow & c_8 & c_8 & c_8 & c_8 & c_7 & c_6 & c_5 & c_4 & c_3 & c_2 & c_1 & c_0 & & & u_1 \\ k = 6: & y_7 & y_6 & y_5 & \Rightarrow & d_8 & d_8 & d_7 & d_6 & d_5 & d_4 & d_3 & d_2 & d_1 & d_0 & & & & u_2 \\ & u_3 \end{array}$$

---

$$p_{15} \quad p_{14} \quad p_{13} \quad p_{12} \quad p_{11} \quad p_{10} \quad p_9 \quad p_8 \quad p_7 \quad p_6 \quad p_5 \quad p_4 \quad p_3 \quad p_2 \quad p_1 \quad p_0$$

Ref: Marco Annaratone, *Digital CMOS Circuit Design*, Kluwer Academic Publishers, 1986.

## Booth Multiplier Verilog Code: Part 1 of 3

```
// behavioral model for a Booth-encoded 8x8 signed multiplier
// 16-bit output => interpreted as a 16-bit signed number
module booth16f(x, y, p);

input  [7:0]  x, y;
output [15:0] p;

reg  [8:0]  a, b, c, d;
reg  u0, u1, u2, u3;
wire [15:0] pp0, pp1, pp2, pp3, pp4;

// perform the booth encoding
always @(x or y) begin
  case (y[1:0])
    2'b00 : begin a = 9'b000000000;      u0 = 0; end // 0
    2'b01 : begin a = {x[7], x[7:0]};    u0 = 0; end // 1
    2'b10 : begin a = {~x[7:0], 1'b1};   u0 = 1; end // -2
    2'b11 : begin a = {~x[7], ~x[7:0]}; u0 = 1; end // -1
  endcase
end
```

## Booth Multiplier Verilog Code: Part 2 of 3

```

case (y[3:1])
  3'b000 : begin b = 9'b000000000;      u1 = 0; end // 0
  3'b001 : begin b = {x[7], x[7:0]};    u1 = 0; end // 1
  3'b010 : begin b = {x[7], x[7:0]};    u1 = 0; end // 1
  3'b011 : begin b = {x[7:0], 1'b0};    u1 = 0; end // 2
  3'b100 : begin b = {~x[7:0], 1'b1};   u1 = 1; end // -2
  3'b101 : begin b = {~x[7], ~x[7:0]}; u1 = 1; end // -1
  3'b110 : begin b = {~x[7], ~x[7:0]}; u1 = 1; end // -1
  3'b111 : begin b = 9'b000000000;      u1 = 0; end // 0
endcase

case (y[5:3])
  3'b000 : begin c = 9'b000000000;      u2 = 0; end // 0
  3'b001 : begin c = {x[7], x[7:0]};    u2 = 0; end // 1
  3'b010 : begin c = {x[7], x[7:0]};    u2 = 0; end // 1
  3'b011 : begin c = {x[7:0], 1'b0};    u2 = 0; end // 2
  3'b100 : begin c = {~x[7:0], 1'b1};   u2 = 1; end // -2
  3'b101 : begin c = {~x[7], ~x[7:0]}; u2 = 1; end // -1
  3'b110 : begin c = {~x[7], ~x[7:0]}; u2 = 1; end // -1
  3'b111 : begin c = 9'b000000000;      u2 = 0; end // 0
endcase

```

## Booth Multiplier Verilog Code: Part 3 of 3

```

case (y[7:5])
    3'b000 : begin d = 9'b000000000;      u3 = 0; end // 0
    3'b001 : begin d = {x[7], x[7:0]};    u3 = 0; end // 1
    3'b010 : begin d = {x[7], x[7:0]};    u3 = 0; end // 1
    3'b011 : begin d = {x[7:0], 1'b0};    u3 = 0; end // 2
    3'b100 : begin d = {~x[7:0], 1'b1};   u3 = 1; end // -2
    3'b101 : begin d = {~x[7], ~x[7:0]}; u3 = 1; end // -1
    3'b110 : begin d = {~x[7], ~x[7:0]}; u3 = 1; end // -1
    3'b111 : begin d = 9'b000000000;      u3 = 0; end // 0
endcase
end

// form the partial product terms
assign pp0 = {a[8], a[8], a[8], a[8], a[8], a[8], a[8], a[8:0]};
assign pp1 = {b[8], b[8], b[8], b[8], b[8], b[8:0], 2'b00};
assign pp2 = {c[8], c[8], c[8], c[8:0], 4'b0000};
assign pp3 = {d[8], d[8:0], 6'b000000};
assign pp4 = {9'b000000000, u3, 1'b0, u2, 1'b0, u1, 1'b0, u0};

// add up the partial product terms
assign p = pp0 + pp1 + pp2 + pp3 + pp4;

endmodule

```

## Booth Multiplier – Exhaustive Testbench: Part 1 of 2

```
module tb16; // testbench for the 8-bit by 8-bit Booth signed multiplier
    // exhaustive checking of all 256*256 possible cases

    reg [7:0] x, y; // 8-bit inputs
    integer xval, yval; // numerical values of inputs x and y
    wire [15:0] p; // 16-bit output of the multiplier circuit
    integer pval; // numerical value of the product
    integer check; // value used to check correctness
    integer i, j; // loop variables
    integer num_correct; // counter to keep track of the number correct
    integer num_wrong; // counter to keep track of the number wrong

    // instantiate the 8-bit by 8-bit radix-4 Booth-encoded signed multiplier
    booth16f mult_instance(x, y, p);

    // exhaustive simulation of all 256*256 = 65,536 possible cases
    initial begin
        // initialize the counter variables
        num_correct = 0; num_wrong = 0;
```



## Booth Multiplier – Exhaustive Testbench: Part 2 of 2

```
// loop through all possible cases and record the results
for (i = 0; i < 256; i = i + 1) begin
  x = i;
  xval = -x[7]*128 + x[6:0];
  for (j = 0; j < 256; j = j + 1) begin
    y = j;
    yval = -y[7]*128 + y[6:0];
    check = xval * yval;

    // compute and check the product
    #10 pval = -p[15]*32768 + p[14:0];
    if (pval == check)
      num_correct = num_correct + 1;
    else
      num_wrong = num_wrong + 1;

    // following line is commented out, but is useful for debugging
    // $display($time, " %d * %d = %d (%d)", xval, yval, pval, check);
  end
end

// print the final counter values
$display("num_correct = %d, num_wrong = %d", num_correct, num_wrong);
end

endmodule
```

## Booth Multiplier – Exhaustive Testbench Results

num\_correct = 65536, num\_wrong = 0

Some results if // is removed

650170	-3 *	-8 =	24 (	24)
650180	-3 *	-7 =	21 (	21)
650190	-3 *	-6 =	18 (	18)
650200	-3 *	-5 =	15 (	15)
650210	-3 *	-4 =	12 (	12)
650220	-3 *	-3 =	9 (	9)
650230	-3 *	-2 =	6 (	6)
650240	-3 *	-1 =	3 (	3)
650250	-2 *	0 =	0 (	0)
650260	-2 *	1 =	-2 (	-2)
650270	-2 *	2 =	-4 (	-4)