
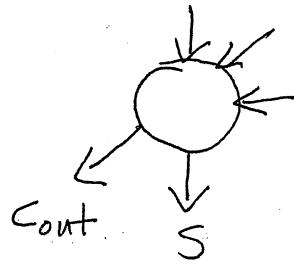


full adder:

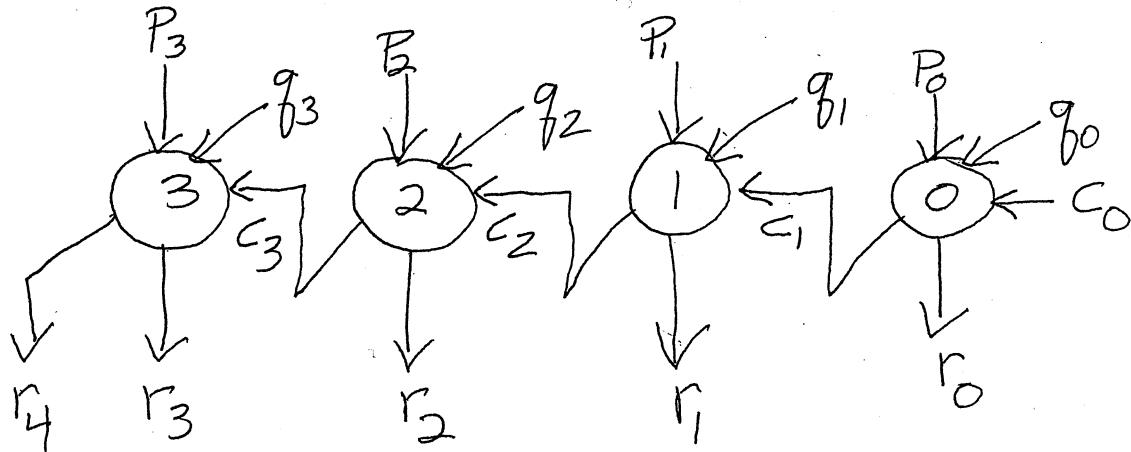

RCA:



```
module full_adder(a, b, cin, s, cout);  
  
    input a, b, cin;  
    output s, cout;  
  
    assign s = a^b^cin;  
    assign cout = (a&b) | (b&cin) | (a&cin);  
  
endmodule  
  
module RCA(p, q, c0, r);  
  
    input [3:0] p, q;  
    input c0;  
    output [4:0] r;  
  
    wire c1, c2, c3;  
  
    full_adder fa0(p[0], q[0], c0, r[0], c1);  
    full_adder fa1(p[1], q[1], c1, r[1], c2);  
    full_adder fa2(p[2], q[2], c2, r[2], c3);  
    full_adder fa3(p[3], q[3], c3, r[3], r[4]);  
  
endmodule
```

file
ripple.v

```

module tb1; // specific input sequence, binary output
reg [3:0] a, b;
reg c;
wire [4:0] s;
// instantiate the 4-bit ripple-carry adder
RCA rcal(a, b, c, s);

```

```

// apply a specific set of input vectors every 10 time units
initial begin

```

```

    a = 4'b0010; b = 4'b1010; c = 1'b0;
#10 a = 4'b1111; b = 4'b0000; c = 1'b0;
#10 a = 4'b0001; b = 4'b0001; c = 1'b1;
end

```

```

// print the input and output values after they change
initial
$monitor($time, " a = %b", a, " b = %b", b, " c = %b", c, " s = %b", s);

```

```

endmodule

```

verilog ripple.v tb1.v

0	a = 0010	b = 1010	c = 0	s = 01100
10	a = 1111	b = 0000	c = 0	s = 01111
20	a = 0001	b = 0001	c = 1	s = 00011

file tb1.v

```

module tb3; // random inputs, decimal values including a check

```

```

reg [3:0] a, b; // 4-bit inputs (to be chosen randomly)
reg c; // carry input (to be chosen randomly)
wire [4:0] s; // 5-bit output of the RCA circuit
reg [4:0] check; // 5-bit sum value used to check correctness

```

```

// instantiate the 4-bit ripple-carry adder
RCA rcal(a, b, c, s);

```

```

// simulation of 20 random addition operations
initial repeat (20) begin

```

```

    // get new operand values and compute a check value
    a = $random; b = $random; c = $random;
    check = a + b + c;

```

file tb3.v

```

    // compute and display the sum every 10 time units
    #10 $display($time, " %d + %d + %d = %d (%d)", a, b, c, s, check);
end

```

```

endmodule

```

verilog ripple.v tb3.v

10	4	+	1	+	1	=	6	(6)
20	3	+	13	+	1	=	17	(17)
30	5	+	2	+	1	=	8	(8)
40	13	+	6	+	1	=	20	(20)
50	13	+	12	+	1	=	26	(26)
60	6	+	5	+	0	=	11	(11)
70	5	+	7	+	0	=	12	(12)
80	15	+	2	+	0	=	17	(17)
90	8	+	5	+	0	=	13	(13)
100	13	+	13	+	1	=	27	(27)
110	3	+	10	+	0	=	13	(13)
120	0	+	10	+	1	=	11	(11)
130	6	+	3	+	1	=	10	(10)
140	3	+	11	+	1	=	15	(15)
150	2	+	14	+	1	=	17	(17)
160	15	+	3	+	0	=	18	(18)
170	10	+	12	+	0	=	22	(22)
180	10	+	1	+	0	=	11	(11)
190	8	+	9	+	1	=	18	(18)
200	6	+	6	+	0	=	12	(12)

```

module tb5; // testbench for signed addition and subtraction

reg [3:0] a, b; // 4-bit inputs (to be chosen randomly)
integer aval, bval; // numerical values of inputs a and b
reg c; // carry input (to be used for subtraction)
wire [4:0] s; // 5-bit output of the RCA circuit
integer sval, dval; // numerical values of the sum and difference
integer sum_check; // value used to check correctness of an addition
integer dif_check; // value used to check correctness of a subtraction

// instantiate the 4-bit ripple-carry adder
RCA rcal(a, b, c, s);

// simulation of 10 additions and 10 subtractions using random operands
initial repeat (10) begin
    // get new operand values and compute the two check values
    a = $random; b = $random; c = 0;
    aval = -a[3]*8 + a[2:0];
    bval = -b[3]*8 + b[2:0];
    sum_check = aval + bval;
    dif_check = aval - bval;

    // compute and display the sum with its check value
    #10 sval = -s[3]*8 + s[2:0];
    $display($time, " %d + %d = %d (%d)", aval, bval, sval, sum_check);

    // compute and display the difference with its check value
    b = ~b; c = 1; // one's complement of b plus 1 into the LSB
    #10 dval = -s[3]*8 + s[2:0];
    $display($time, " %d - %d = %d (%d)", aval, bval, dval, dif_check);
end

endmodule

```

verilog_ripple.v tb5.v

10	4 +	1 =	5 (5)
20	4 -	1 =	3 (3)
30	-7 +	3 =	-4 (-4)
40	-7 -	3 =	6 (-10) ←
50	-3 +	-3 =	-6 (-6)
60	-3 -	-3 =	0 (0)
70	5 +	2 =	7 (7)
80	5 -	2 =	3 (3)
90	1 +	-3 =	-2 (-2)
100	1 -	-3 =	4 (4)
110	6 +	-3 =	3 (3)
120	6 -	-3 =	-7 (9) ←
130	-3 +	-4 =	-7 (-7)
140	-3 -	-4 =	1 (1)
150	-7 +	6 =	-1 (-1)
160	-7 -	6 =	3 (-13) ←
170	5 +	-6 =	-1 (-1)
180	5 -	-6 =	-5 (11) ←
190	5 +	7 =	-4 (12) ←
200	5 -	7 =	-2 (-2)

(arrows show instances of signed overflow)

$$(aval = -a_3 2^3 + \sum_{i=0}^2 a_i 2^i)$$

file
tb5.v

```
// half adder component used in the multiplier
module half_adder(a, b, s, cout);
```

```
    input a, b;
    output s, cout;
```

```
    assign s = a^b;
    assign cout = a&b;
```

```
endmodule
```

```
// full adder component used in the multiplier
module full_adder(a, b, cin, s, cout);
```

```
    input a, b, cin;
    output s, cout;
```

```
    assign s = a^b^cin;
    assign cout = (a&b) | (b&cin) | (a&cin);
```

```
endmodule
```

```
// 3-bit by 3-bit unsigned multiplier
module mult3(x, y, p);
```

```
    input [2:0] x, y;
    output [5:0] p;
```

```
    // internal nodes within the multiplier circuit
    wire t1, t2, t3, t4, t5, t6, t7;
```


```
    // structural description of the multiplier circuit
    assign p[0] = x[0]&y[0];
    half_adder ha1(x[1]&y[0], x[0]&y[1], p[1], t1);
    half_adder ha2(x[2]&y[0], x[1]&y[1], t2, t3);
    full_adder fa1(t2, t1, x[0]&y[2], p[2], t4);
    full_adder fa2(x[2]&y[1], t3, x[1]&y[2], t5, t6);
    half_adder ha3(t5, t4, p[3], t7);
    full_adder fa3(x[2]&y[2], t6, t7, p[4], p[5]);
```

```
endmodule
```

file
mult3.v

$$\begin{array}{r}
 \begin{array}{ccc} x_2 & x_1 & x_0 \\ y_2 & y_1 & y_0 \end{array} \\
 \hline
 \begin{array}{ccc} x_2y_0 & x_1y_0 & x_0y_0 \\ x_2y_1 & x_1y_1 & x_0y_1 \\ \hline x_2y_2 & x_1y_2 & x_0y_2 \end{array} \\
 \hline
 \begin{array}{cccccc} p_5 & p_4 & p_3 & p_2 & p_1 & p_0 \end{array}
 \end{array}$$

3-bit by 3-bit
unsigned
multiplier

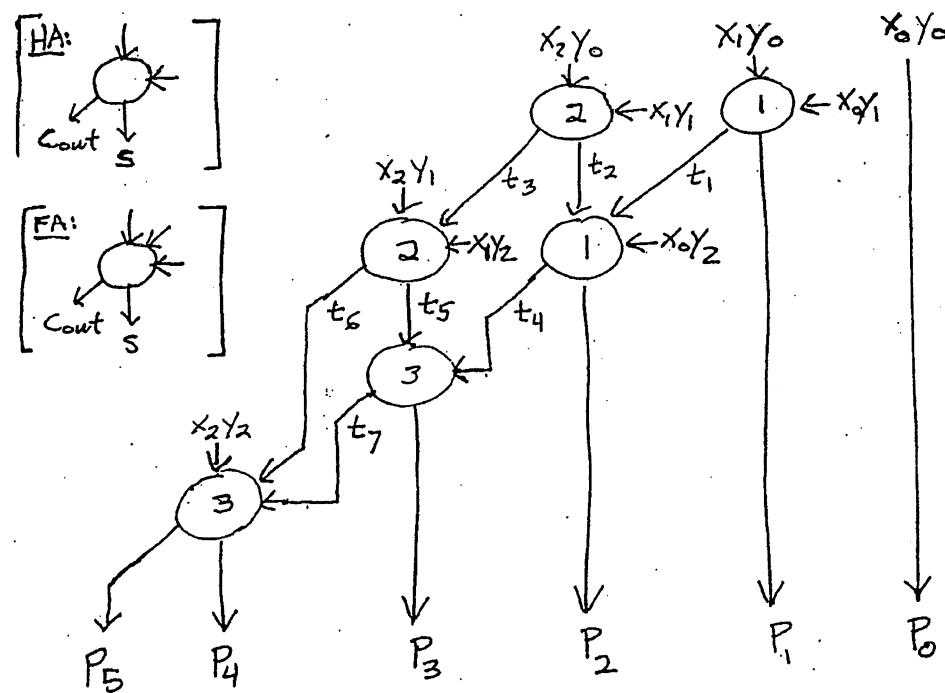

file tb7.v

```

module tb7; // testbench for the 3-bit by 3-bit multiplier
            // random inputs, decimal values including a check

reg [2:0] x, y; // 3-bit inputs (to be chosen randomly)
wire [5:0] p; // 6-bit output of the multiplier circuit
reg [5:0] check; // 6-bit product value used to check correctness

// instantiate the 3-bit by 3-bit multiplier
mult3 mult_instance(x, y, p);

// simulation of 20 random multiplication operations
initial repeat (20) begin
    // get new operand values and compute a check value
    x = $random; y = $random;
    check = x * y;

    // compute and display the product every 10 time units
    #10 $display($time, " %d * %d = %d (%d)", x, y, p, check);
end

endmodule

```

```

module tbe; // testbench for the 3-bit by 3-bit unsigned multiplier
            // exhaustive checking of all 64 possible cases

```

```

reg [2:0] x, y; // 3-bit inputs
wire [5:0] p; // 6-bit output of the multiplier circuit
reg [5:0] check; // 6-bit product value used to check correctness
integer i, j; // loop variables
integer num_correct; // counter to keep track of the number correct
integer num_wrong; // counter to keep track of the number wrong

```

```

// instantiate the 3-bit by 3-bit multiplier
mult3 mult_instance(x, y, p);

// exhaustive checking of all 64 possible cases
initial begin
    // initialize the counter variables
    num_correct = 0; num_wrong = 0;

    // loop through all possible cases and record the results
    for (i = 0; i < 8; i = i + 1) begin
        x = i;
        for (j = 0; j < 8; j = j + 1) begin
            y = j;
            check = x * y;

            // compute and check the product
            #10 if (p == check)
                num_correct = num_correct + 1;
            else
                num_wrong = num_wrong + 1;

            // following line is commented out, but is useful for debugging
            // $display($time, " %d * %d = %d (%d)", x, y, p, check);
        end
    end

    // print the final counter values
    $display("num_correct = %d, num_wrong = %d", num_correct, num_wrong);
end

```

```

endmodule

```

verilog mult3.v tbe.v

num_correct = 64, num_wrong = 0

verilog mult3.v tb7.v

10	4 * 1 = 4	(4)
20	1 * 3 = 3	(3)
30	5 * 5 = 25	(25)
40	5 * 2 = 10	(10)
50	1 * 5 = 5	(5)
60	6 * 5 = 30	(30)
70	5 * 4 = 20	(20)
80	1 * 6 = 6	(6)
90	5 * 2 = 10	(10)
100	5 * 7 = 35	(35)
110	2 * 7 = 14	(14)
120	2 * 6 = 12	(12)
130	0 * 5 = 0	(0)
140	4 * 5 = 20	(20)
150	5 * 5 = 25	(25)
160	3 * 2 = 6	(6)
170	0 * 0 = 0	(0)
180	2 * 5 = 10	(10)
190	6 * 3 = 18	(18)
200	5 * 3 = 15	(15)

file tbe.v